

2. Superconducting circuits for QIP


Freitag, 21. Oktober 2011

09:34

2.1. Parallel LC circuit - harmonic oscillator

Mittwoch, 21. März 2012
12:50

parallel LC oscillating circuit:

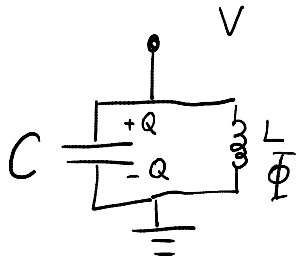

Voltage across oscillator:

$$V = \frac{Q}{C} = - \frac{d\Phi}{dt} = -L \frac{dI}{dt}$$

energy stored in the circuit: (Hamiltonian)

$$H = \underbrace{\frac{1}{2} \cdot C V^2}_{\text{capacitive (electrostatic) energy}} + \underbrace{\frac{1}{2} L I^2}_{\text{inductive (magnetic) energy}} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} \frac{\Phi^2}{L}$$

Φ ... magnetic flux stored in the inductor ($\Phi = LI$)



Q ... charge stored on the capacitor ($Q = CV$)

↑ canonical variables

$$\left[\begin{array}{l} \frac{\partial H}{\partial Q} = \frac{Q}{C} = -L \frac{\partial I}{\partial t} = -\dot{\Phi} \\ \frac{\partial H}{\partial \Phi} = \frac{\Phi}{L} = I = \dot{Q} \end{array} \right]$$

mechanical harmonic oscillator:
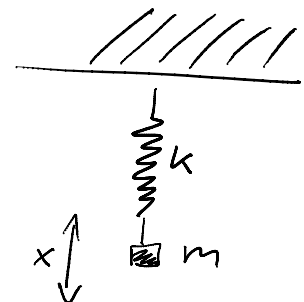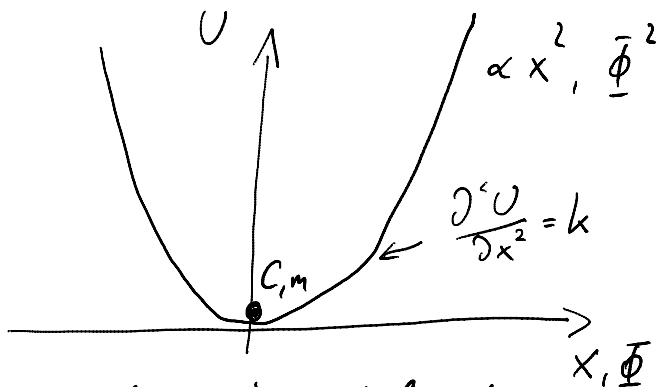
$$H = \underbrace{\frac{p^2}{2m}}_{\text{kinetic energy}} + \underbrace{\frac{k}{2} x^2}_{\text{potential energy}}$$



(virtual) particle of mass m (C) moving in potential

Characteristic quantities:

mechanical

position x

momentum p

mass m

spring constant k

frequency $\omega = \sqrt{\frac{k}{m}}$

electronic

flux Φ

charge Q

capacitance C

inverse inductance $\frac{1}{L}$

$$\omega = \frac{1}{\sqrt{LC}}$$

H0

} canonical variables

2.2. Quantum harmonic oscillator

Mittwoch, 21. März 2012

12:54

$$x \rightarrow \hat{x}$$

$$p \rightarrow \hat{p} = -i\hbar \frac{\partial}{\partial x}$$

$$\Phi \rightarrow \hat{\Phi}$$

$$Q \rightarrow \hat{Q} = -i\hbar \frac{\partial}{\partial \Phi}$$

Commutation relations:

$$[\hat{x}, \hat{p}] = i\hbar$$

$$[\hat{\Phi}, \hat{Q}] = i\hbar \quad \text{flux-charge} \quad | \cdot \frac{1}{\hbar}$$

$$\Leftrightarrow \left[2\pi \frac{\Phi}{\Phi_0}, \frac{\hat{Q}}{2e} \right] = [\hat{J}, \hat{N}] = i \quad \text{phase-number}$$

Φ_0 ... magnetic flux quantum $\frac{h}{2e}$

Hamilton operator

$$H = \frac{\hat{Q}^2}{2C} + \frac{\hat{\Phi}^2}{2L}$$

creation and annihilation operators


$$\hat{a}^{\dagger} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q}^{\dagger} - i \hat{\Phi}^{\dagger}) \quad \text{creation operator}$$

$$\hat{a} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q} + i \hat{\Phi}) \quad \text{annihilation operator}$$

$$Z_c = \sqrt{\frac{L}{C}}, \quad \omega = \frac{1}{\sqrt{LC}} \quad \text{impedance, resonance freq.}$$

$$\Rightarrow \hat{H} = \hbar\omega \left(\hat{a}^{\dagger} \hat{a} - \frac{1}{2} \right) \quad \hat{a}^{\dagger} \hat{a} \dots \text{number operator}$$

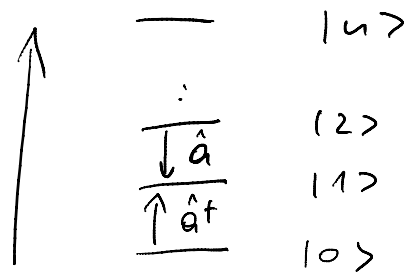energy level spectrum
 equidistant level
 spacing



properties

$$\hat{a}^\dagger |n\rangle = \sqrt{n+1} |n+1\rangle$$

$$\hat{a} |n\rangle = \sqrt{n} |n-1\rangle$$

$$\hat{a}^\dagger \hat{a} |n\rangle \equiv \hat{n} |n\rangle = n |n\rangle$$

$|n\rangle \dots$ Fock state with
 n excitations

relation to \hat{Q} , $\hat{\Phi}$ & \hat{V} , \hat{I} (inverse relations)

$$\hat{Q} = \sqrt{\frac{\hbar}{2Z_c}} (\hat{a}^\dagger + \hat{a}) \quad \hat{\Phi} = i \sqrt{\frac{\hbar Z_c}{2}} (\hat{a}^\dagger - \hat{a})$$

$$\text{or } \hat{V} = \frac{\hat{Q}}{C} = \sqrt{\frac{\hbar C}{2C^2 L}} (\hat{a}^\dagger + \hat{a}) = \sqrt{\frac{\hbar \omega}{2C}} (\hat{a}^\dagger + \hat{a})$$


$$\hat{I} = \frac{\hat{\Phi}}{L} = i \sqrt{\frac{\hbar \omega}{2L}} (\hat{a}^\dagger - \hat{a}) \quad \left[\omega = \frac{1}{LC} \right]$$

2.3. Transmission line resonator


Mittwoch, 21. März 2012

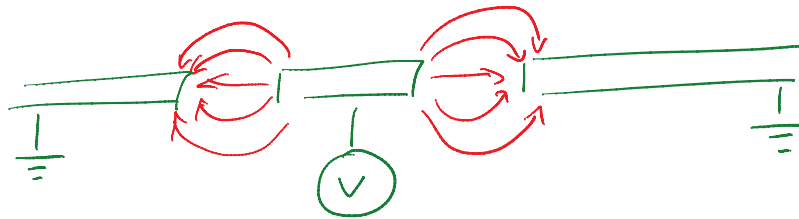12:56


Field distribution of the transmission line?



Wave propagation in a transmission line?

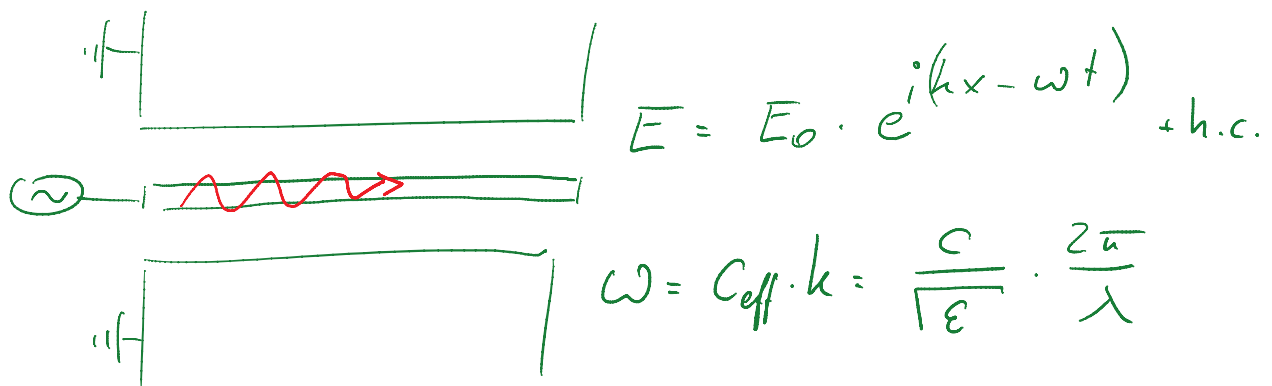


Electric field at the boundary?

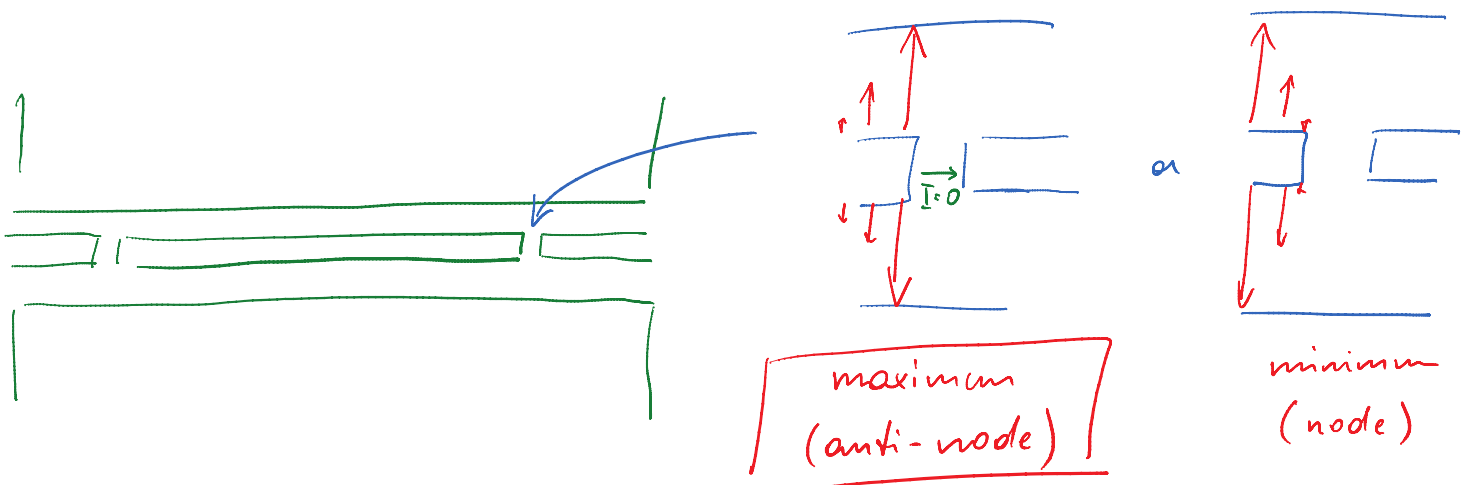

no current \Rightarrow voltage maximum \Rightarrow field maximum


Fundamental mode?

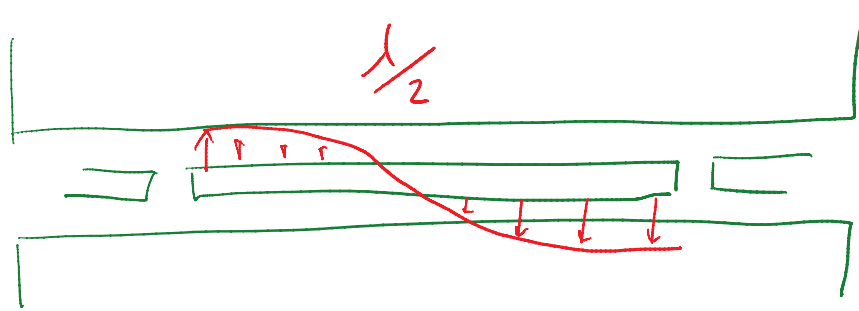

Resonance frequency?

$$\left. \begin{aligned} \omega &= c_{\text{eff}} \frac{2\pi}{\lambda} \\ l &= \frac{\lambda}{2} \cdot n \end{aligned} \right\} \omega = c_{\text{eff}} \frac{2\pi}{2l} = \frac{\pi c_{\text{eff}}}{l} \cdot n$$

Excitation spectrum:

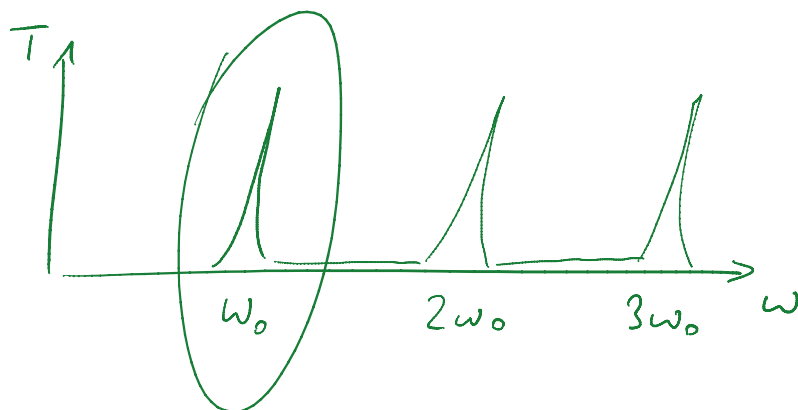

↳ harmonic oscillator
photons $\hat{=}$ excitation quanta


2.4. Josephson Junction as non-linear inductor

Mittwoch, 21. März 2012

12:58

induction law: $V = -L \dot{I}$

Josephson relation: $I = I_0 \cdot \sin \delta$ | dc |
 (supercurrent across junction)

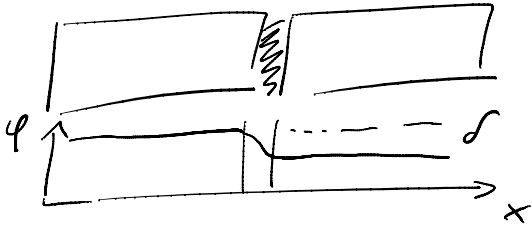

$V = \frac{\phi_0}{2\pi} \dot{\delta}$ | ac |

(time-dependent phase if voltage is applied)

$$\dot{I} = I_0 \cdot \cos \delta \dot{\delta} \quad \Rightarrow \quad V = \frac{\phi_0}{2\pi I_0} \frac{1}{\cos \delta} \dot{I} \equiv L_J \dot{I}$$

Josephson Inductance:

$$L_J = L_{J0} \left(\frac{1}{\cos \delta} \right) \rightarrow \text{non-linearity}$$

$$L_{J0} = \frac{\phi_0}{2\pi I_0} \text{ specific Josephson inductance}$$

Josephson Energy: $E_J = \int V I dt' = \int \frac{\phi_0 I_0}{2\pi} \dot{\delta} \sin \delta dt'$

$$= \int \frac{\phi_0 I_0}{2\pi} \sin \delta d\delta = \frac{\phi_0 I_0}{2\pi} \cos \delta$$

$$= E_{J0} \cos \delta \text{ with } E_{J0} = \frac{\phi_0 I_0}{2\pi}$$

Typical parameters:

$$\bar{I}_0 = 100 \text{ nA}$$

$$\Rightarrow L_{30} = \frac{\phi_0}{2\pi \bar{I}_0} \approx 3 \text{ nH} \quad (\sim 3 \text{ mm of wire})$$

$$\Rightarrow E_{30} = \frac{\phi_0 \bar{I}_0}{2\pi} \approx 50 \text{ GHz}$$